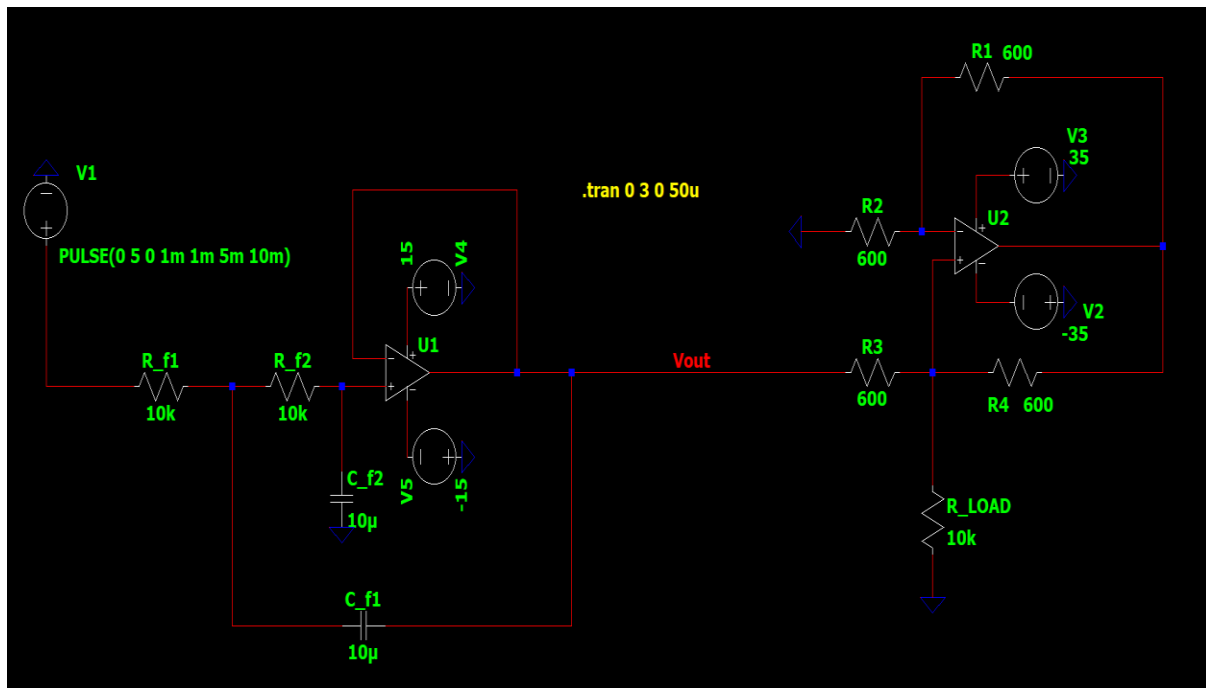



Voltage-Controlled Current Source (VCCS) Design – Simulation Results

CIRCUIT DIAGRAM :-




Filtering Of PWM :-

- 60% Duty Cycle at 100Hz
- 0-5V PWM

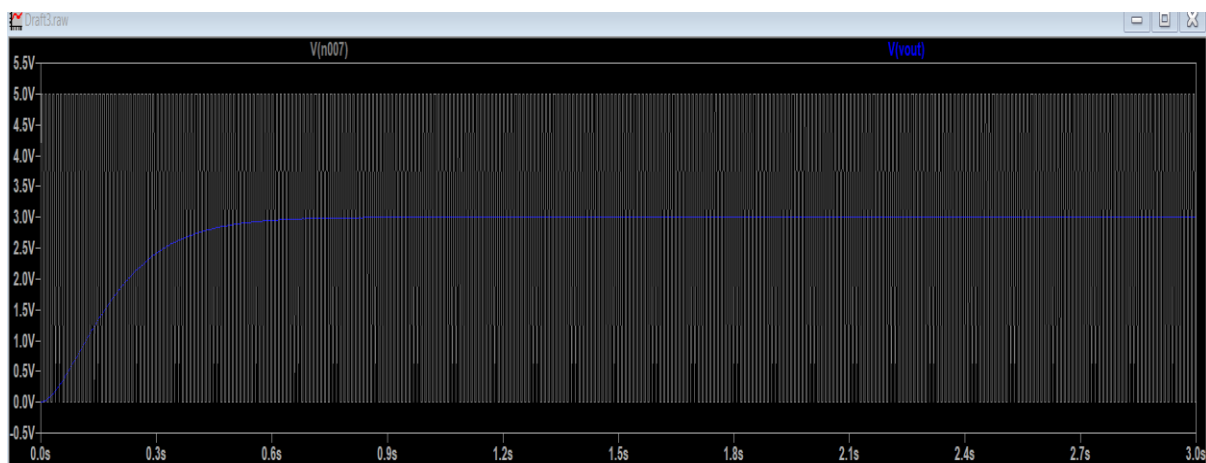


Output Current for $R_{load} = 1k\Omega$:-

- 0-5V PWM and 100Hz

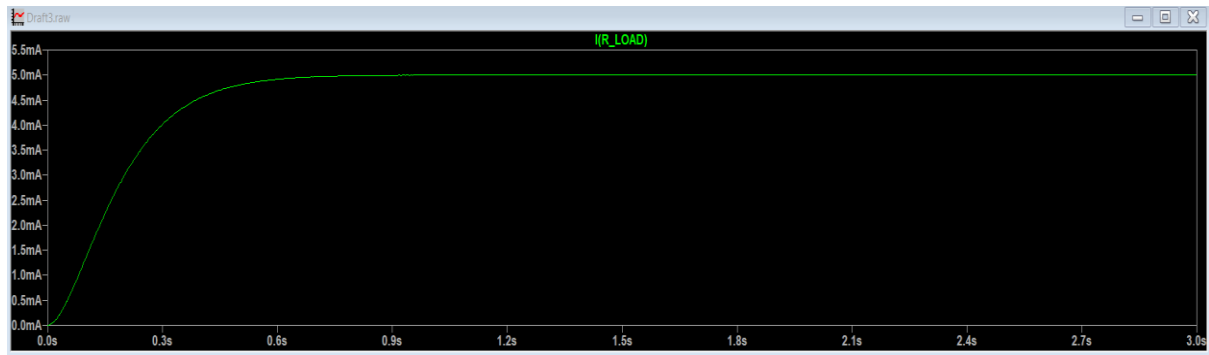


Output Current for $R_{load} = 5k\Omega$:-

- 0-5V PWM and 100Hz

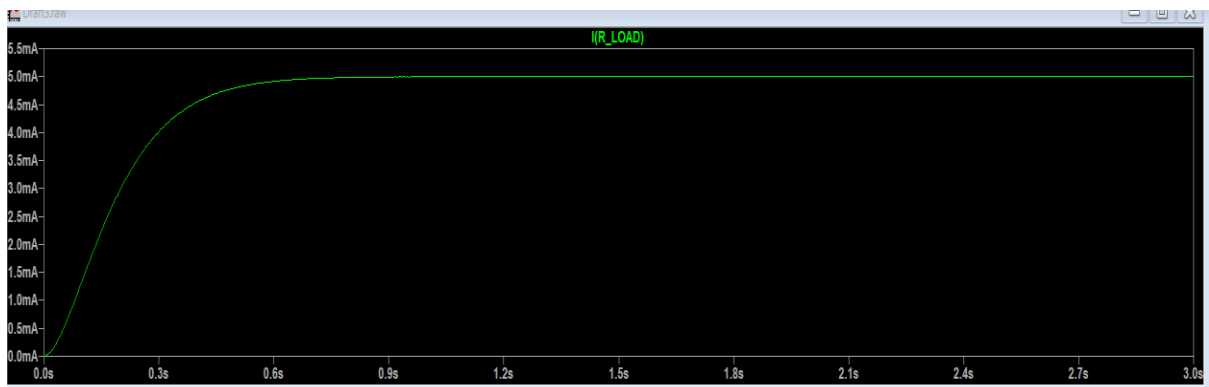


Output Current for $R_{load} = 10k\Omega$:-

- 0-5V PWM and 100Hz

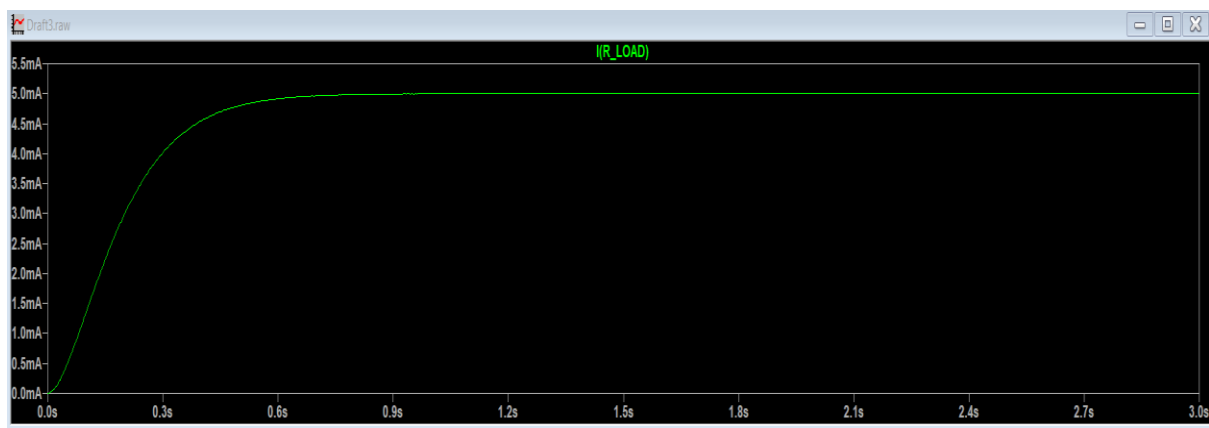


Output Current for PWM Frequency = 20Hz :-

- 0-5V PWM

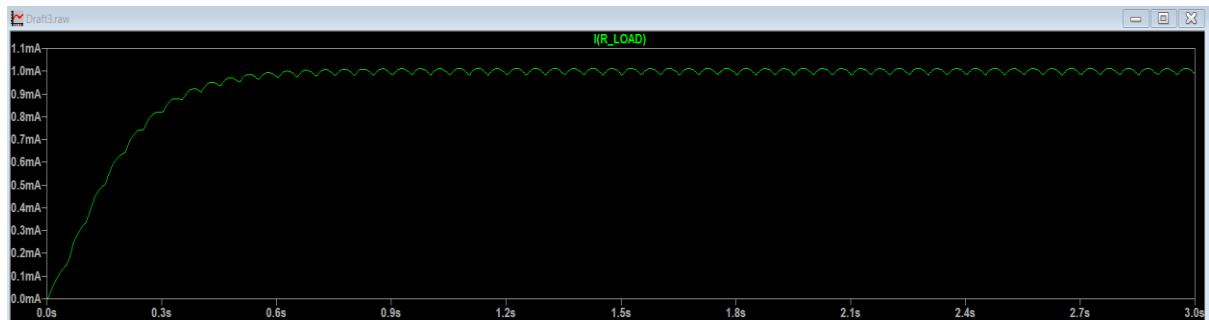

Output Current for PWM Frequency = 100Hz :-

- 0-5V PWM

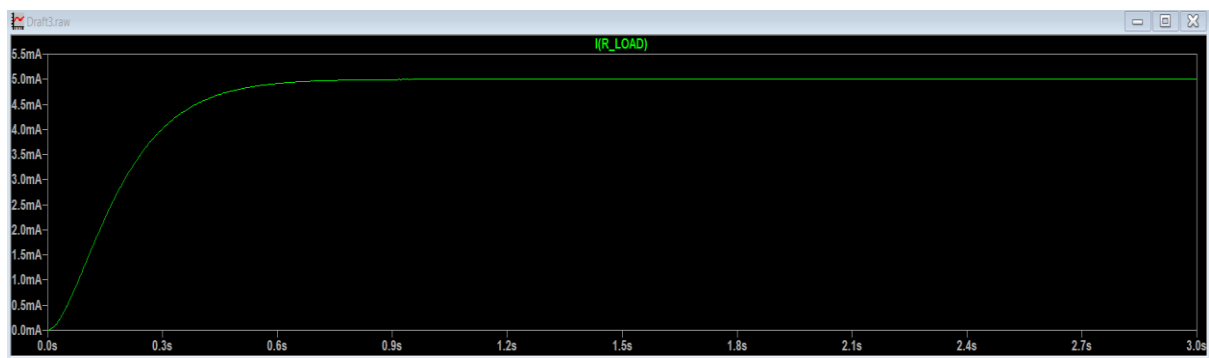

Output Current for PWM Frequency = 200Hz :-

- 0-5V PWM

